

Memory Interface

In this chapter, we explain how to interface both ROM and RAM to the Intel family of microprocessors.

Memory Devices and Interface, Chapter 10

Slide 1

Objectives

- Upon completion of this chapter, you will be able to
 - Decode the memory address and use the outputs of the decoder to select various memory components.
 - Use programmable logic devices to decode memory addresses.
 - Explain how to interface both ROM and RAM to a microprocessor.
 - Interface memory to an 8-, 16-, 32- and 64-bit data bus.
 - Explain the operation of a dynamic RAM controller.
 - Interface dynamic RAM to the microprocessor.


Memory Devices and Interface, Chapter 10

Slide 2

Memory Devices

Memory Pin Connections:

- Address connections:
 - Address inputs that select a memory location within the memory device.
- Data connections:
 - Data outputs or input/outputs at which data are entered for storage or extracted for reading.
- Selection connections:
 - Signal inputs that selects or enables the memory device. (e.g. chip enable \overline{CE} , chip select \overline{CS} , select S etc.)
- Control connections:
 - Signal inputs that controls the operation of the memory device (e.g. write enable \overline{WE} , read enable \overline{RE} , output enable \overline{OE} , read/write R/\overline{W} etc.)

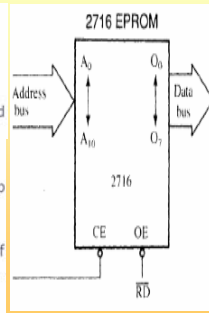

Memory Devices and Interface, Chapter 10

Slide 3

Memory Devices

ROM Memory:

- The **read-only memory (ROM)** is permanently programmed so data are always present, even when power is disconnected.
- It is used to store programs and data that are resident to the system and must not change when power is disconnected.
- It is also called **nonvolatile memory**.
- The **EPROM (erasable programmable ROM)** is erasable if exposed to high-intensity ultraviolet light for about minutes.
- The **PROM (programmable ROM)** is programmed in the field by burning open tiny fuses, but once programmed it can't be erased.

Memory Devices and Interface, Chapter 10

Slide 4

Memory Devices

ROM Memory:

- The **EEPROM (electrically erasable programmable ROM)** is electrically erasable in the system, but require more time to erase than a normal RAM.
- EEPROM is also called **flash memory**.
- This type of memory component requires wait states to operate properly with the 8088/8086 processors because of its rather long access time.

Memory Devices and Interface, Chapter 10

Slide 5

Memory Devices

Static RAM:


- It **retains data for as long as DC power is applied**.
- No special action (except power) is required to retain stored data.
- The access time of a SRAM is much shorter than that of a ROM, and no wait state is required in general.
- Examples include 4016(2K×8) and 62256(32K×8).

Memory Devices and Interface, Chapter 10

Slide 6

Address Decoding

- Use PROM decoder:

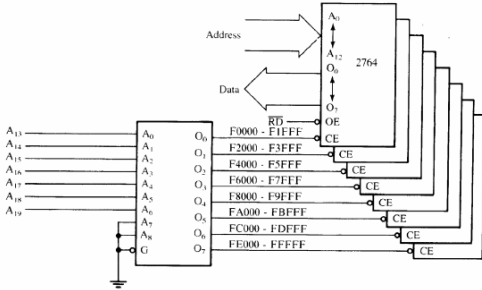

A memory system using the TPB26L42, 512 x 8 PROM as an address

Memory Devices and Interface, Chapter 10

Slide 13

Address Decoding

The 825147 PROM programming pattern for the illustrated circuit.

Inputs								Outputs									
OE	A8	A7	A6	A5	A4	A3	A2	A1	A0	O0	O1	O2	O3	O4	O5	O6	O7
0	0	0	1	1	1	1	0	0	0	1	0	1	1	1	1	1	1
0	0	0	1	1	1	1	0	0	1	1	0	1	1	1	1	1	1
0	0	0	1	1	1	1	0	1	0	1	1	0	1	1	1	1	1
0	0	0	1	1	1	1	0	1	1	1	1	0	1	1	1	1	1
0	0	0	1	1	1	1	1	0	0	1	1	1	1	0	1	1	1
0	0	0	1	1	1	1	1	0	1	1	1	1	1	1	0	1	1
0	0	0	1	1	1	1	1	1	0	1	1	1	1	1	1	0	1
0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0
0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
all other combinations										1	1	1	1	1	1	1	1


Memory Devices and Interface, Chapter 10

Slide 14

Address Decoding


- Use PLD programmable decoders:

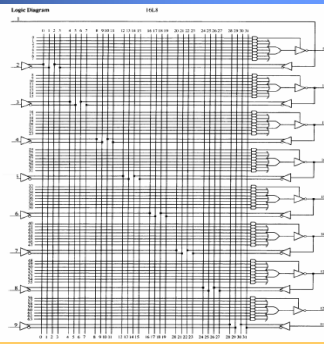The PAL 16L8
(Advanced Micro Devices, Inc., 1988.)



Memory Devices and Interface, Chapter 10

Slide 15

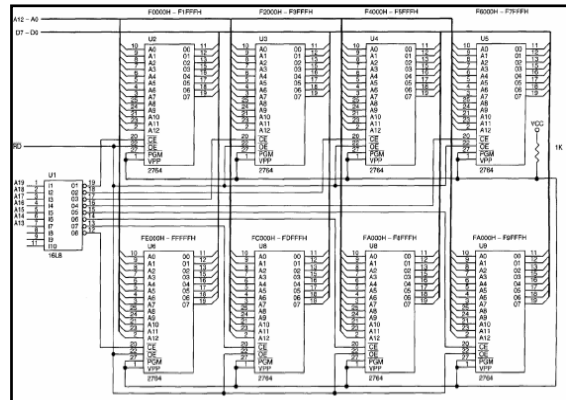


A PAL16L8 that decodes 8 2764 (8K x 8) memory devices

Memory Devices and Interface, Chapter 10

Slide 16

Address Decoding Example

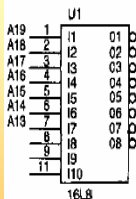

```

TITLE      Address Decoder
CHIP      DECODER1 PAL16L8

:pins 1 2 3 4 5 6 7 8 9 10
      A19 A18 A17 A16 A15 A14 A13 NC NC GND


:pins 11 12 13 14 15 16 17 18 19 20
      NC O8 O7 O6 O5 O4 O3 O2 O1 VCC

EQUATIONS

/O1 = A19 * A18 * A17 * A16 * /A15 * /A14 * /A13
/O2 = A19 * A18 * A17 * A16 * /A15 * /A14 * A13
/O3 = A19 * A18 * A17 * A16 * /A15 * A14 * /A13
/O4 = A19 * A18 * A17 * A16 * /A15 * /A14 * A13
/O5 = A19 * A18 * A17 * A16 * A15 * /A14 * /A13
/O6 = A19 * A18 * A17 * A16 * A15 * A14 * /A13
/O7 = A19 * A18 * A17 * A16 * A15 * /A14 * A13
/O8 = A19 * A18 * A17 * A16 * A15 * /A14 * A13
    
```

Memory Devices and Interface, Chapter 10

Slide 17

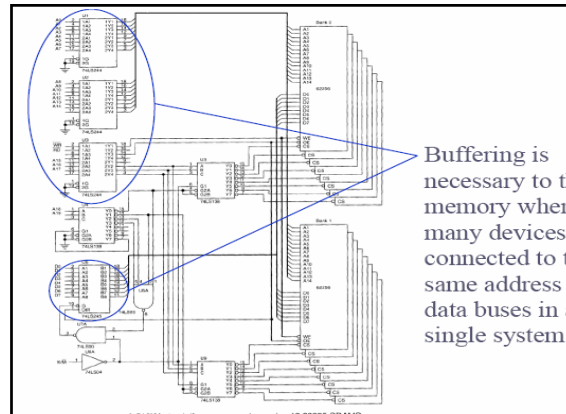

Buffering is necessary to the memory when many devices are connected to the same address and data buses in a single system.

A 512K byte static memory system using 16 82255 SRAMs

Memory Devices and Interface, Chapter 10

Slide 18


Interfacing Flash Memory to CPU

- Differences between a flash memory device and SRAM
 - the flash memory device requires a 12 V programming voltage (V_{pp}) to erase and write new data
 - the amount of time required to accomplish a write operation ($\sim 0.4s$ in flash memory c.w. $\sim 10ns$ in SRAM)

Memory Devices and Interface, Chapter 10

Slide 19

Interfacing Flash Memory to CPU

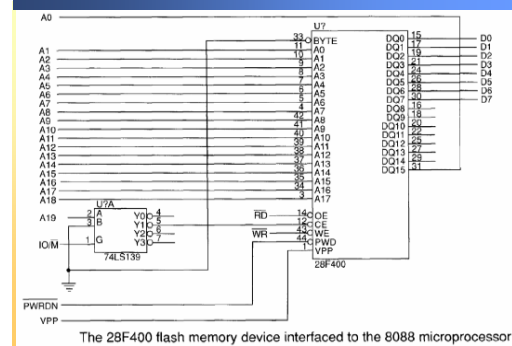

The 28F400 flash memory device interfaced to the 8088 microprocessor

Memory Devices and Interface, Chapter 10

Slide 20


Interfacing Flash Memory to CPU

- The Intel 28F400 flash memory device can be used as either a 512Kx8 (byte mode) memory device or as a 256Kx16 (word mode) memory device, which is selected by the control pin BYTE.
- The pin DQ15 of 28F400 functions as the least significant address input when the device operates in the byte mode.

Memory Devices and Interface, Chapter 10

Slide 21

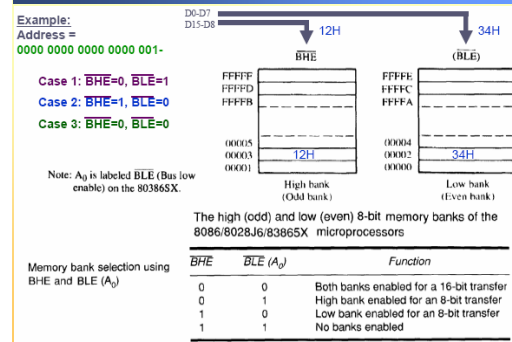
16-bit Memory Interface (8086/80286/80386SX)



Memory Devices and Interface, Chapter 10

Slide 22

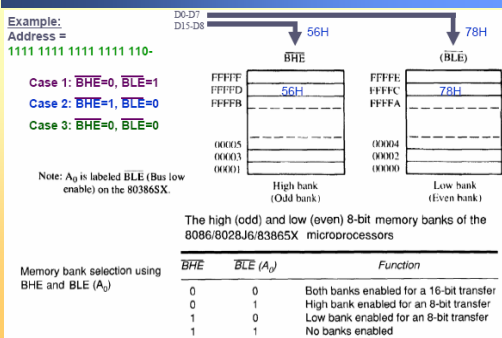16-bit Memory Interface (8086/80286/80386SX)



Memory Devices and Interface, Chapter 10

Slide 23

16-bit Memory Interface (8086/80286/80386SX)

- Bank selection can be accomplished in two ways:
 - Issue a separate write signal to select a write to each bank of memory.
 - Use separate decoders for each bank.
- No separate read signal is required for each memory bank as processors can select the data they need at any time from half of the data bus.

Memory Devices and Interface, Chapter 10

Slide 24

16-bit Memory Interface (8086/80286/80386SX)

Separate Bank Decoders:


- It's more expensive and less effective.

Example:
Address =
0000 1110 0000 0000 0000 0000

Case 1: BHE=0, BLE=1

Case 2: BHE=1, BLE=0


Case 3: BHE=0, BLE=0

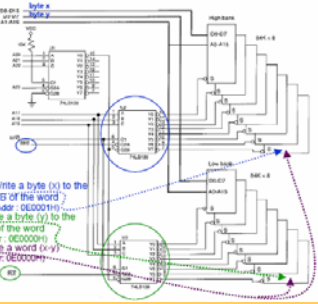

Memory Devices and Interface, Chapter 10

Slide 25

Example of a 16-bit Memory Interface

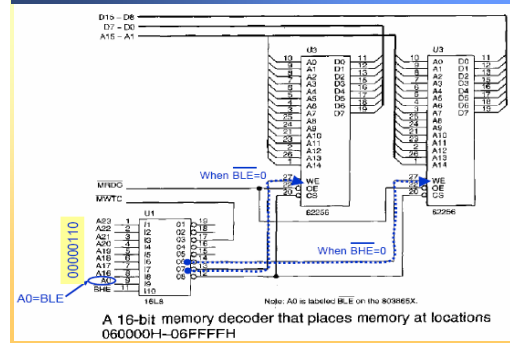


Memory Devices and Interface, Chapter 10

Slide 26

16-bit Memory Interface (8086/80286/80386SX)

Separate Bank Write Strobes:

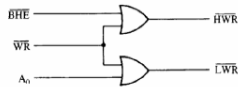- It's more effective and less expensive.



```


TITLE      Address Decoder
CHIP      DECODER2 PAL16L8
;pins 1 2 3 4 5 6 7 8 9 10
A23 A22 A21 A20 A19 A18 A17 A16 A0 GND
;pins 11 12 13 14 15 16 17 18 19 20
BHE SEL LWR HWR NC NC MWTC NC NC VCC

EQUATIONS
/SEL = /A23 * /A22 * /A21 * /A20 * /A19 * A18 * A17 * /A16
/LWR = /MWTC * /A0
/HWR = /MWTC * /BHE
    
```

Memory Devices and Interface, Chapter 10

Slide 27

Example of a 16-bit Memory Interface

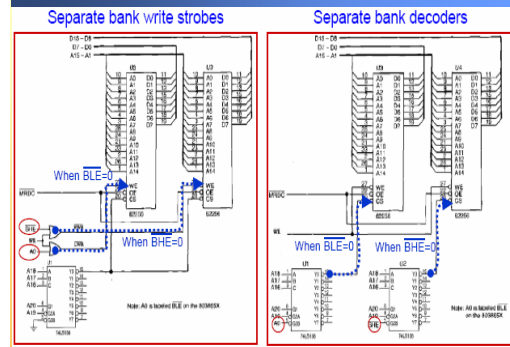


Memory Devices and Interface, Chapter 10

Slide 28

32-bit Memory Interface (80386DX and 80486)

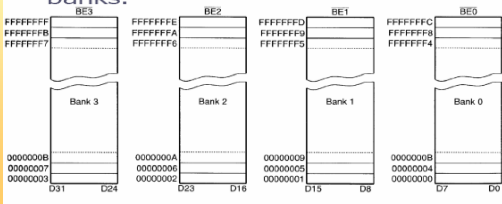- Bank selection can be accomplished by the bank selection signals $\overline{BE3}$, $\overline{BE2}$, $\overline{BE1}$ and $\overline{BE0}$.
- A 8-, 16- or 32-bit number can be transferred by selecting appropriate banks.




Memory Devices and Interface, Chapter 10

Slide 29

32-bit Memory Interface (80386DX and 80486)


- Separate write strobe signals can be developed to select a write to each memory bank.

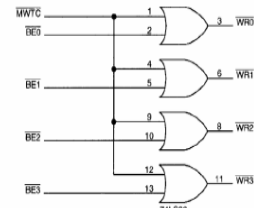Bank write signals for the 80386DX and 80486 microprocessors



Memory Devices and Interface, Chapter 10


Slide 30

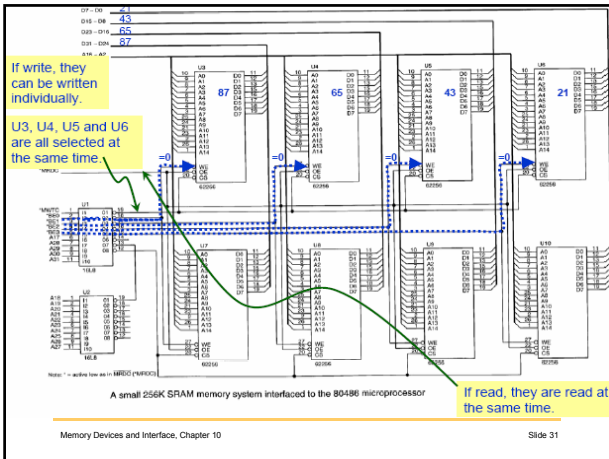

64-bit Memory Interface (Pentium Processors)

- Bank selection is accomplished by the bank selection signals $\overline{BE7}$, $\overline{BE6}$, $\overline{BE5}$, $\overline{BE4}$, $\overline{BE3}$, $\overline{BE2}$, $\overline{BE1}$ and $\overline{BE0}$.
- A 8-, 16-, 32- or 64-bit number can be transferred by selecting appropriate banks.

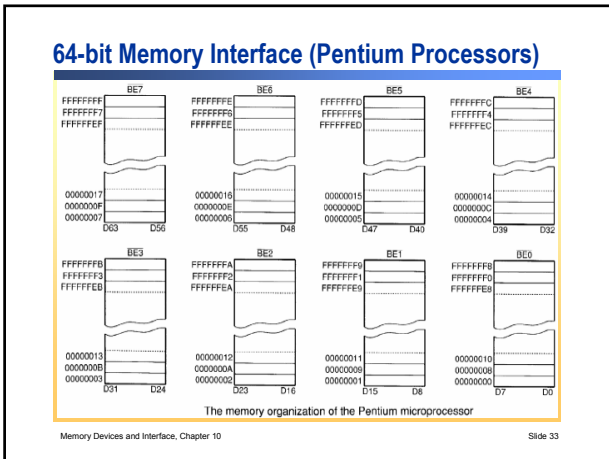Memory Devices and Interface, Chapter 10 Slide 32




64-bit Memory Interface (Pentium Processors)

The separate write strobe signals can be obtained by combining the bank selection signals with the /MWTC signal, which is generated by combining the M/I/O and W/R.

The generation of the write strobes for the Pentium microprocessor

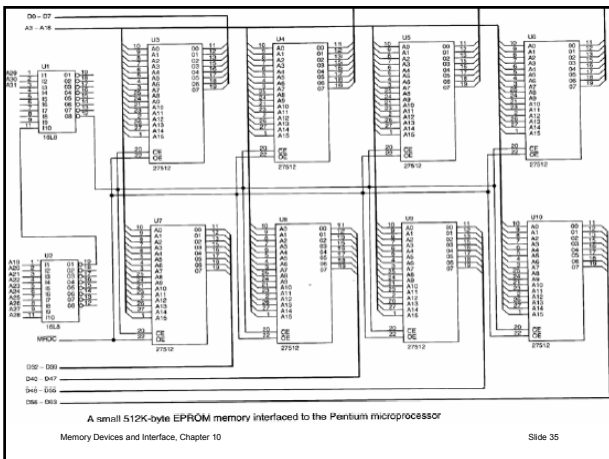Memory Devices and Interface, Chapter 10 Slide 34



Dynamic RAM

- As RAM memory is often very large, sometimes it is desirable to use DRAMs instead of SRAMs to **reduce the system cost**.
- A DRAM **retains data for only 2-4 ms** and **requires the multiplexing of address inputs**.
- DRAM **must be refreshed periodically**.

Memory Devices and Interface, Chapter 10 Slide 36


Dynamic RAM

- A refresh can be accomplished by doing a read, a write, or a special refresh cycle that doesn't read or write data.
- A refresh cycle which is totally internal to the DRAM is called either **hidden refresh**, **transparent refresh**, or sometimes **cycle stealing**.
- In a **hidden refresh**, an RAS-only cycle strobes a row address into the DRAM to select a row of bits to be refreshed, and, at the same time, the RAS input also causes the selected row to be read out internally and rewritten into the selected bits.

Memory Devices and Interface, Chapter 10

Slide 37

Internal Structure of a Dynamic RAM

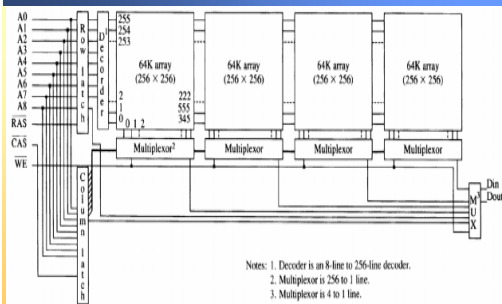


The internal structure of a 256K x 1 DRAM. Note that each of the internal 256 words are 1,025-bits wide.

Memory Devices and Interface, Chapter 10

Slide 38

- Step 1: Give a 9-bit row addr (e.g. 0 1111 1110B)
Step 2: Give a 9-bit col addr (e.g. 1 0000 0001B)
Step 3: Get a bit

Read Example

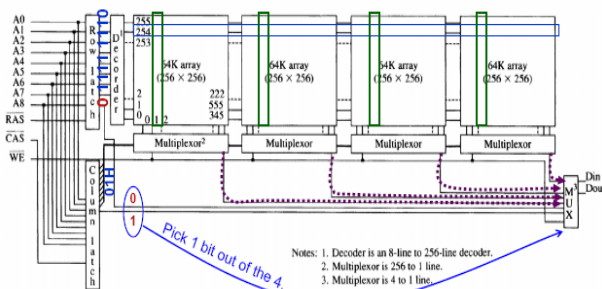


The internal structure of a 256K x 1 DRAM. Note that each of the internal 256 words are 1,025-bits wide.

Memory Devices and Interface, Chapter 10

Slide 39

Refresh Example

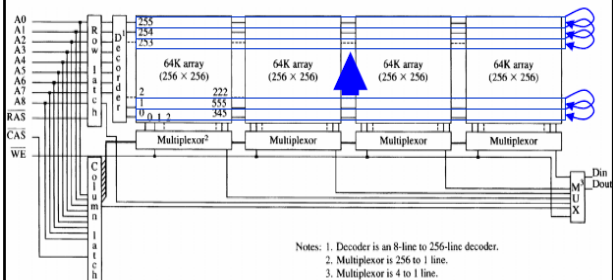- Step 0: DRAM controller initializes ROW addr counter = 0
Step 1: Give a 9-bit row addr by a DRAM controller
Step 2: read & write the row internally
Step 3: the DRAM controller increases the ROW addr by 1
Step 4: IF ROW addr < 256 GOTO step 1, else GOTO step 0



The internal structure of a 256K x 1 DRAM. Note that each of the internal 256 words are 1,025-bits wide.

Memory Devices and Interface, Chapter 10

Slide 40

Refresh Overhead

- The row address is usually obtained from a binary counter.
- An **overhead is required** to perform the refresh when exploiting the DRAM.
- In a 8088/8086 system running at a **5 MHz** clock, it takes **800 ns** to do a refresh.
- If there are **256 rows** to be refreshed within **4 ms**, then the refresh cycle must be activated at least once every $4\text{ms}/256 = 15.6\mu\text{s}$ to meet the specification.
- In other words, it takes 800ns to refresh every 15.6ms.
- Hence, the **overhead** = $0.8/15.6 \approx 5.13\%$.

Memory Devices and Interface, Chapter 10

Slide 41

Refresh Overhead

- In a modern microprocessors such as a **3.0 GHz Pentium IV**, the period of **15.6μs** is a great deal of time!
- Since this **Pentium IV** executes an instruction in about **one-third ns**, the refreshment overhead is much less than 1%, as shown below:

$$\text{Overhead Time}\% = \frac{0.333 \text{ ns}}{15.6 \mu\text{s}} \times 100\% = \frac{111}{52000}\%$$

$$\text{Overhead Time}\% \approx 0.0021\%$$

Memory Devices and Interface, Chapter 10

Slide 42

EDO Memory

- EDO (Extended data Output) RAM is a modified version of DRAM. In this type of memory, any memory access, including a refresh, stores the selected row of bits into latches. Thus, in most programs, which are sequentially executed, the row of latched data are available without any wait states.
- This slight modification to the internal architecture of the DRAM increases system performance by about 15 to 25%.
- Although EDO memory is no longer available, this technique is still employed in all modern DRAM chips (SDRAM and DDRAM).

Memory Devices and Interface, Chapter 10

Slide 43

The Intel 82C08 DRAM Controller

- The Intel 82C08 DRAM controller can control up to 2 banks of 256Kx16 DRAM memory (i.e. 1M byte of memory).
- The 82C08 contains an address multiplexer that multiplexes an 18-bit address onto 9 address connections for 256K memory devices and circuitry that generates $\overline{\text{RAS}}$ and $\overline{\text{CAS}}$ signals for the DRAM.

5	AL0	AD0	7
6	AL1	AD1	8
7	AL2	AD2	9
318	AL313	AD313	320